

Chapter 5


2 Port Network

Lecture 3

For the circuit shown below, the input


$$\text{resistance } R_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} \text{ is}$$

[GATE IN 2008, IISc Bangalore]

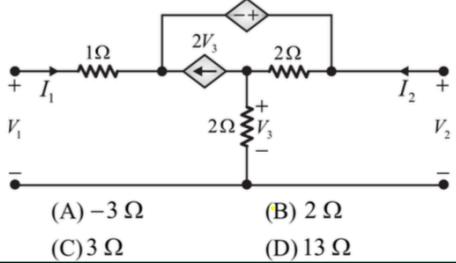

(A) -3Ω
 (C) 3Ω

Digitized by srujanika@gmail.com

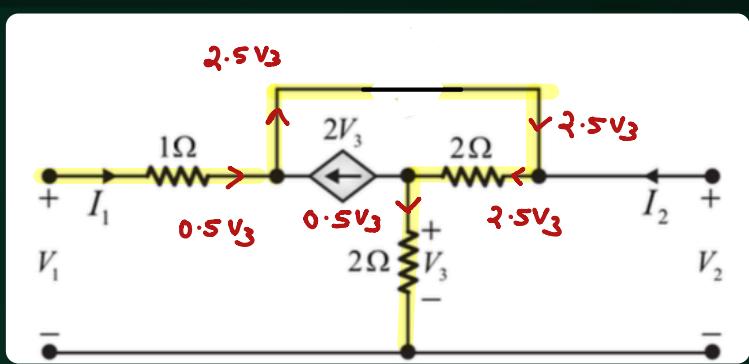

$$I_1 = 0.5 V_3$$


$$v_1 = (0.5v_3)(1) + (2.5v_3)(2) + (0.5v_3)3$$

$$V_1 = 6.5 V_3$$

$$\therefore \frac{V_1}{I_1} = \frac{6.5V_3}{0.5V_3} = \underline{\underline{13}} \text{~N}$$

The ABCD parameters of the following 2-port network are

[GATE EC 2015 (Set 03), IIT Kanpur]

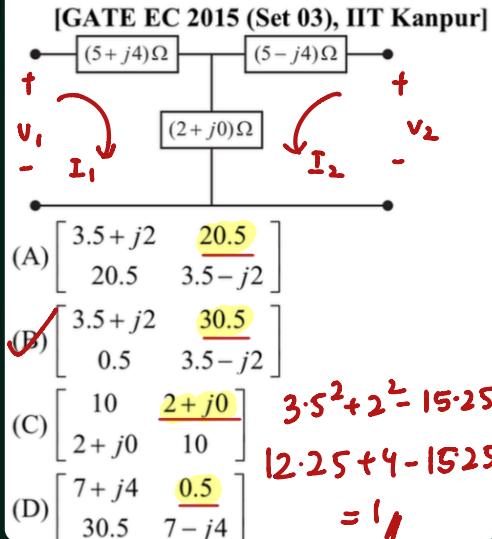

Method ①

$$V_1 = (7 + j4)I_1 + 2I_2$$

$$V_2 = 2I_1 + (7-j4)I_2$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

$$V_1 = A V_2 - B I_2$$

$$\therefore B = \frac{V_1}{-I_2} \Big|_{V_2=0}$$

$$-2x_1 = (7 - j4)x_2$$

$$\therefore I_1 = \frac{(7-j4)}{-2} I_2$$


Subs in ①

$$V_1 = \frac{(7+j4)(7-j4) I_2}{-2} + 2I_2$$

$$V_1 = \left(\frac{49 + 16}{-2} \right) I_2 + 2 I_2 = -30.5 I_2$$


$$\Rightarrow B = \frac{V_1}{-I_2} = 30.5$$

Interconnection of 2 port Networks

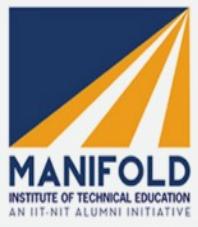


Rules

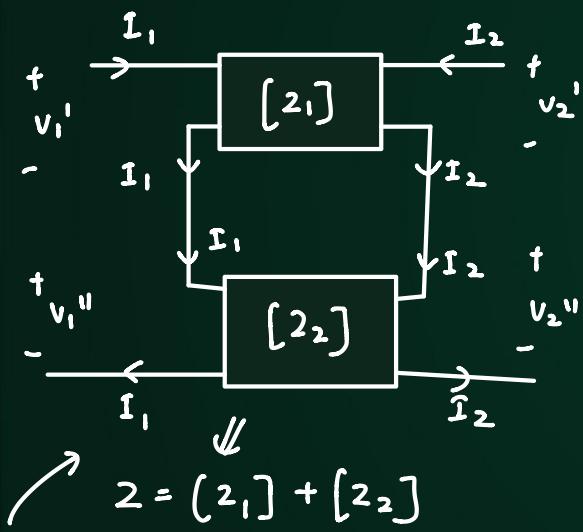
- ① Series \longrightarrow 2 parameters are added
 - ② Parallel \longrightarrow Y parameters are added
 - ③ Cascade \longrightarrow ABCD parameters are multiplied.



Series Interconnection

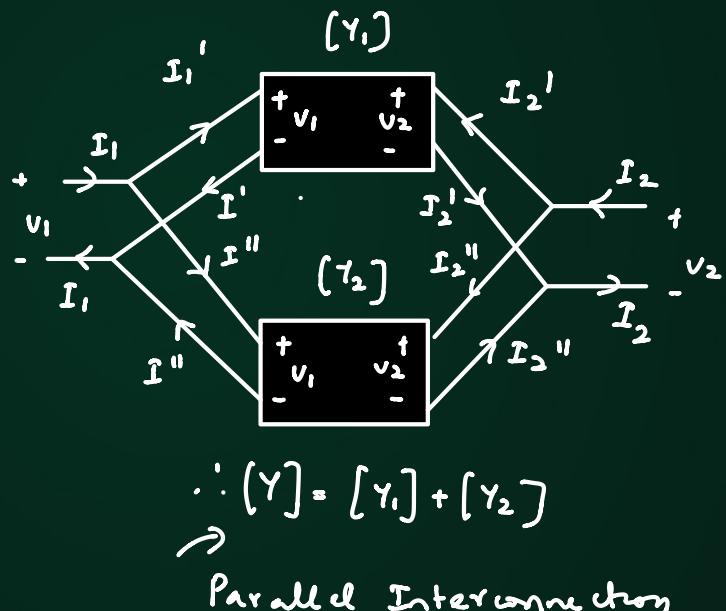


Cascade Interconnection

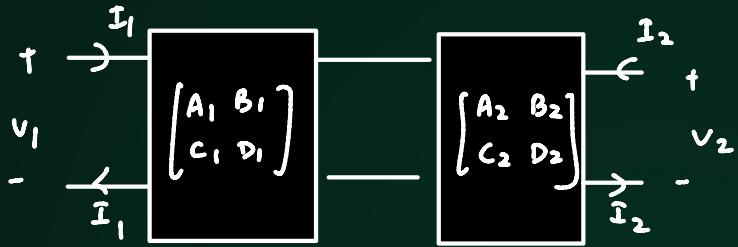

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix}$$

Two passive two-port networks are connected in cascade as shown in figure. A voltage source is connected at port 1.

[GATE EE 2017 (Set - 01), IIT Roorkee]

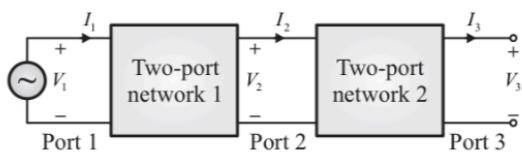

Given :

$$\begin{aligned} V_1 &= A_1V_2 + B_1I_2 & I_1 &= C_1V_2 + D_1I_2 \\ V_2 &= A_2V_3 + B_2I_3 & I_2 &= C_2V_3 + D_2I_3 \end{aligned}$$

$A_1, B_1, C_1, D_1, A_2, B_2, C_2$ and D_2 are the generalized circuit constants. If the Thevenin equivalent circuit at port 3 consists of a voltage source V_T and an impedance Z_T connected in series, then

V_T : Thevenin voltage

$$V_T = V_3 \mid_{I_3=0}$$

$$R_{41} = \frac{V_3}{-I_3} \Big|_{V_1=0} \quad \text{when } I_3 = 0$$


www.manifoldkerala.com

- (A) $V_T = \frac{V_1}{A_1 A_2}$, $Z_T = \frac{A_1 B_2 + B_1 D_2}{A_1 A_2 + B_1 C_2}$

(B) $V_T = \frac{V_1}{A_1 A_2 + B_1 C_2}$, $Z_T = \frac{A_1 B_2 + B_1 D_2}{A_1 A_2}$

(C) $V_T = \frac{V_1}{A_1 + A_2}$, $Z_T = \frac{A_1 B_2 + B_1 D_2}{A_1 + A_2}$

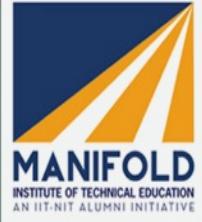(D) $V_T = \frac{V_1}{A_1 A_2 + B_1 C_2}$, $Z_T = \frac{A_1 B_2 + B_1 D_2}{A_1 A_2 + B_1 C_2}$



$$\begin{bmatrix} U_1 \\ I_1 \end{bmatrix} = \underbrace{\begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix}}_{\text{Matrix } M_1} \underbrace{\begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix}}_{\text{Matrix } M_2} \begin{bmatrix} U_3 \\ I_3 \end{bmatrix}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} A_1 A_2 + B_1 C_2 & \underline{B_1 D_2} \\ \underline{-} & \underline{-} \end{bmatrix}$$

$$\therefore V_1 = AV_3 + BI_3 \quad | \textcircled{1}$$

$$\Leftrightarrow I_1 = C v_3 + D I_3$$


$$V_3 = \frac{V_1}{A} \quad \text{or} \quad V_3 = \frac{C}{I_1}$$

$$V_3 = \frac{V_1}{A_1 A_2 + B_1 C_2} = V_T$$

From ① when $V_1 = 0$

$$AV_3 = -BI_3$$

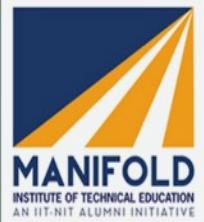
$$\therefore \frac{V_3}{-I_3} = R_M = \frac{B}{A} = \frac{A_1 B_2 + B_1 D_2}{A_1 A_2 + B_1 C_2}$$



The connection of two 2-port networks is shown in the figure. The ABCD parameters of N_1 and N_2 networks are given as

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix}_{N_1} = \begin{bmatrix} 1 & 5 \\ 0 & 1 \end{bmatrix} \text{ and}$$
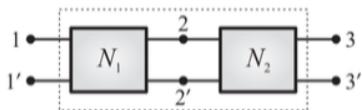
$$\begin{bmatrix} A & B \\ C & D \end{bmatrix}_{N_2} = \begin{bmatrix} 1 & 0 \\ 0.2 & 1 \end{bmatrix}$$




The ABCD parameters of the combined 2-port network are

- | | |
|--|--|
| (A) $\begin{bmatrix} 2 & 5 \\ 0.2 & 1 \end{bmatrix}$ | (B) $\begin{bmatrix} 1 & 2 \\ 0.5 & 1 \end{bmatrix}$ |
| (C) $\begin{bmatrix} 5 & 2 \\ 0.5 & 1 \end{bmatrix}$ | (D) $\begin{bmatrix} 1 & 2 \\ 0.5 & 5 \end{bmatrix}$ |



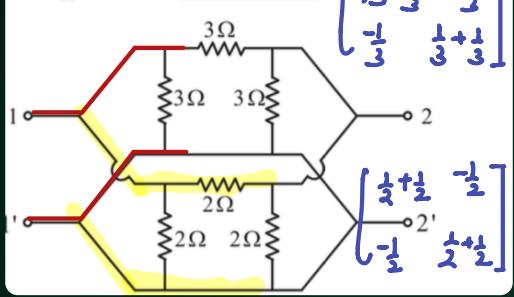In the h-parameter model of the 2-port network given in the figure shown, the value of h_{22} (in S) is _____.



$$[Y] = \begin{bmatrix} 5/3 & -5/6 \\ -5/6 & 5/3 \end{bmatrix}$$

$$\begin{cases} I_1 = \frac{5}{3}V_1 - \frac{5}{6}V_2 & \textcircled{1} \\ I_2 = -\frac{5}{6}V_1 + \frac{5}{3}V_2 & \textcircled{2} \end{cases}$$

$$\frac{5}{6} v_2 = \frac{5}{3} v_1$$

$$V_1 = 0.5 V_2$$

Subs in ②

$$I_2 = -\frac{5}{6} \left(\frac{1}{2} v_2 \right) + \frac{5}{3} v_2 = -\frac{5}{12} v_2 + \frac{20}{12} v_2 = \frac{15}{12} v_2$$

$$h_{22} = \frac{I_2}{V_2} = \underline{\underline{\frac{5}{4}}}$$

Rule : Y parameters can be added


$$Y = \begin{pmatrix} \frac{2}{3} + 1 & -\frac{5}{6} \\ -\frac{5}{6} & \frac{2}{3} + 1 \end{pmatrix}$$

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

$$I_2 = h_{21} I_1 + h_{22} v_2$$

$$\therefore h_{22} = \frac{I_2}{V_2} \Big|_{I_1=0}$$

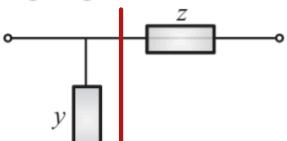Which one of the following is the transmission matrix for the network shown in the figure given below?



$$(A) \begin{bmatrix} 1 & 1+yz \\ y & z \end{bmatrix}$$

$$3) \begin{bmatrix} 1+yz & z \\ y & 1 \end{bmatrix}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ Y & 1 \end{bmatrix} \begin{bmatrix} 1 & 2 \\ 0 & 1 \end{bmatrix}$$

$$= \begin{pmatrix} 1 & 2 \\ Y & 1+Y^2 \end{pmatrix}$$




MANIFOLD
INSTITUTE OF TECHNICAL EDUCATION
AN IIT-NIT ALUMNI INITIATIVE


ABCD


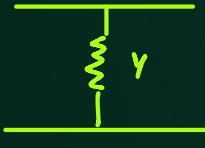
$$\begin{bmatrix} 1 & 2 \\ 0 & 1 \end{bmatrix}$$


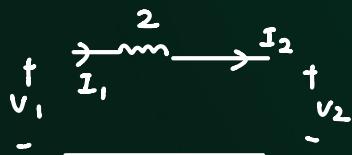
$$\begin{bmatrix} i & o \\ y & i \end{bmatrix}$$



$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$


$$V_1 = V_2 + 2 I_2 \quad (2)$$

$$\begin{pmatrix} v_1 \\ I_1 \end{pmatrix} = \begin{pmatrix} 1 & 2 \\ 0 & 1 \end{pmatrix} \begin{pmatrix} v_2 \\ I_2 \end{pmatrix}$$

In the arrangement of figure given below

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} 30 & 23 \\ 13 & 10 \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

ABCD parameter of Network N_0 is

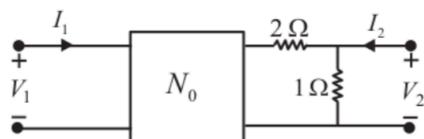

- (A) $\begin{bmatrix} 7 & -9 \\ 3 & -4 \end{bmatrix}$ (B) $\begin{bmatrix} 7 & 9 \\ 3 & 4 \end{bmatrix}$
 (C) $\begin{bmatrix} -7 & 9 \\ 3 & -4 \end{bmatrix}$ (D) $\begin{bmatrix} 1 & 2 \\ 3 & 4 \end{bmatrix}$

$$\begin{bmatrix} 30 & 23 \\ 13 & 10 \end{bmatrix} = \begin{bmatrix} a & b \\ c & d \end{bmatrix} \begin{bmatrix} 1 & 2 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 1 & 1 \end{bmatrix}$$

$$\begin{bmatrix} 30 & 23 \\ 13 & 10 \end{bmatrix} = \begin{bmatrix} a & b \\ c & d \end{bmatrix} \begin{bmatrix} 3 & 2 \\ 1 & 1 \end{bmatrix} = \begin{bmatrix} \underline{3a+b} & \underline{2a+b} \\ \underline{3c+d} & \underline{2c+d} \end{bmatrix}$$

$$a = 30 - 23 = 7 \quad b = 9 \\ c = 13 - 10 = 3 \quad d = 4 \quad \begin{bmatrix} 7 & 9 \\ 3 & 4 \end{bmatrix} \quad (B)$$