

## Chapter 5

### 2 Port Network


---

### Lecture 3

For the circuit shown below, the input

resistance  $R_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0}$  is

[GATE IN 2008, IISc Bangalore]

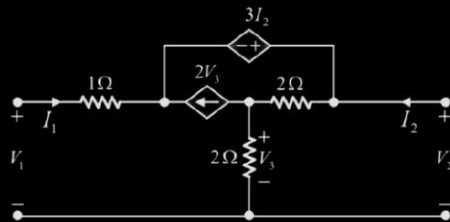


(A)  $-3 \Omega$

(B)  $2 \Omega$

(C)  $3 \Omega$

(D)  $13 \Omega$

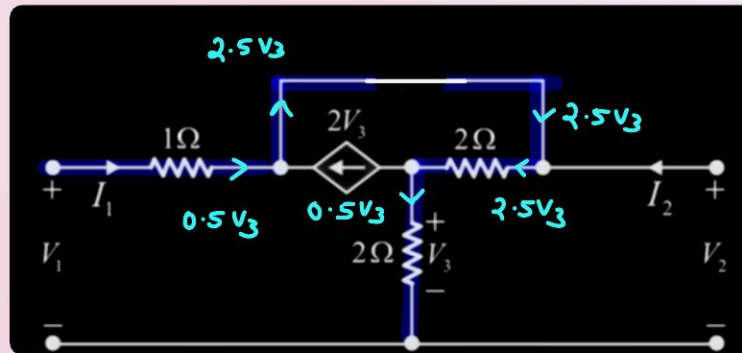

$$I_1 = 0.5V_3$$


$$V_1 = (0.5V_3)(1) + (2.5V_3)(2) + (0.5V_3)2$$

$$V_1 = 6.5V_3$$

$$\therefore \frac{V_1}{I_1} = \frac{6.5V_3}{0.5V_3} = \underline{\underline{13 \Omega}}$$

The ABCD parameters of the following 2-port network are

[GATE EC 2015 (Set 03), IIT Kanpur]

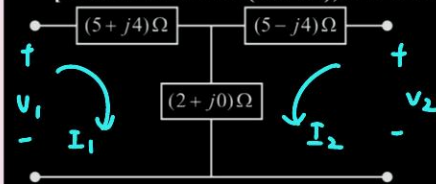

(A)  $\begin{bmatrix} 3.5+j2 & 20.5 \\ 20.5 & 3.5-j2 \end{bmatrix}$

(B)  $\begin{bmatrix} 3.5+j2 & 30.5 \\ 0.5 & 3.5-j2 \end{bmatrix}$

(C)  $\begin{bmatrix} 10 & 2+j0 \\ 2+j0 & 10 \end{bmatrix}$

(D)  $\begin{bmatrix} 7+j4 & 0.5 \\ 30.5 & 7-j4 \end{bmatrix}$

$3 \cdot 5^2 + 2^2 = 15.25$   
 $12 \cdot 2.5 + 4 - 15.25 = 1$

Method ①

$$V_1 = (7+j4)I_1 + 2I_2$$

$$V_2 = 2I_1 + (7-j4)I_2$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

$$V_1 = AV_2 - BI_2$$

$$\therefore B = \frac{V_1}{-I_2} \bigg|_{V_2=0}$$

$$-2I_1 = (7-j4)I_2$$

$$\therefore I_1 = \frac{(7-j4)I_2}{-2}$$

Subs in ①

$$V_1 = \frac{(7+j4)(7-j4)I_2}{-2} + 2I_2$$


$$V_1 = \left( \frac{49+16}{-2} \right) I_2 + 2I_2 = -30.5I_2$$

$$B = \frac{V_1}{-I_2} = 30.5$$

# Interconnection of 2 port Networks

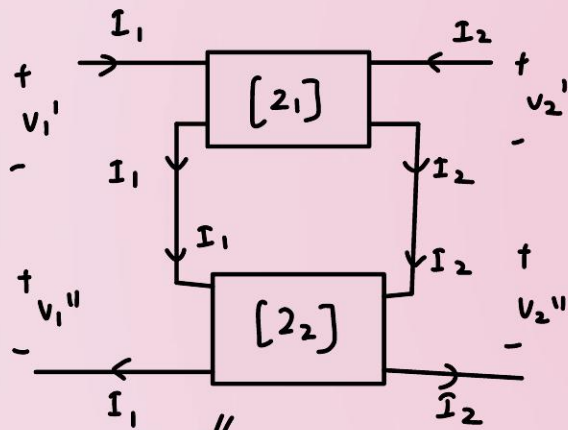
## Rules

- ① Series  $\longrightarrow$  2 parameters are added
- ② Parallel  $\longrightarrow$  Y parameters are added
- ③ Cascade  $\longrightarrow$  ABCD parameters are multiplied.



$$Z = [Z_1] + [Z_2]$$


Series Interconnection

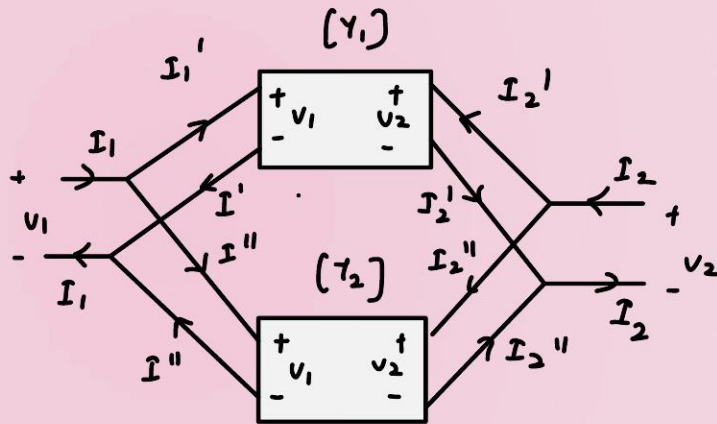

$$\therefore [Y] = [Y_1] + [Y_2]$$

Parallel Interconnection


## Cascade Interconnection

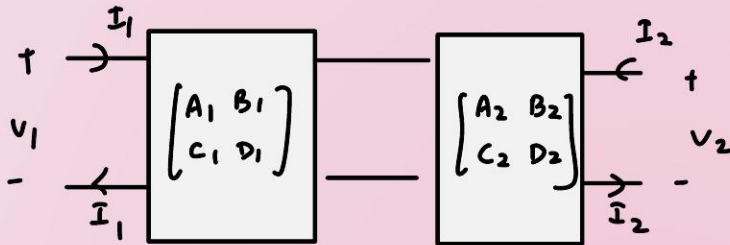

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix}$$

Two passive two-port networks are connected in cascade as shown in figure. A voltage source is connected at port 1.

[GATE EE 2017 (Set - 01), IIT Roorkee]

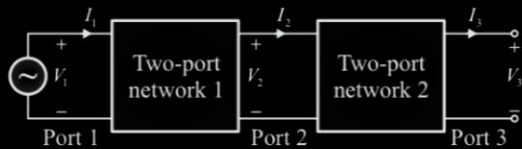

Given :

$$V_1 = A_1 V_2 + B_1 I_2 \quad I_1 = C_1 V_2 + D_1 I_2$$

$$V_2 = A_2 V_3 + B_2 I_3 \quad I_2 = C_2 V_3 + D_2 I_3$$

$A_1, B_1, C_1, D_1, A_2, B_2, C_2$  and  $D_2$  are the generalized circuit constants. If the Thevenin equivalent circuit at port 3 consists of a voltage source  $V_T$  and an impedance  $Z_T$  connected in series, then

$V_T$ : Thevenin voltage

$$V_T = V_3 \big|_{I_3 = 0}$$

$$R_{Th} = \frac{V_3}{-I_3} \big|_{V_1 = 0} \quad \text{When } I_3 = 0$$

$$(A) V_T = \frac{V_1}{A_1 A_2}, \quad Z_T = \frac{A_1 B_2 + B_1 D_2}{A_1 A_2 + B_1 C_2}$$

$$(B) V_T = \frac{V_1}{A_1 A_2 + B_1 C_2}, \quad Z_T = \frac{A_1 B_2 + B_1 D_2}{A_1 A_2}$$

$$(C) V_T = \frac{V_1}{A_1 + A_2}, \quad Z_T = \frac{A_1 B_2 + B_1 D_2}{A_1 + A_2}$$

$$(D) V_T = \frac{V_1}{A_1 A_2 + B_1 C_2}, \quad Z_T = \frac{A_1 B_2 + B_1 D_2}{A_1 A_2 + B_1 C_2}$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} \begin{bmatrix} V_3 \\ I_3 \end{bmatrix}$$

$$\Downarrow$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} A_1 A_2 + B_1 C_2 & A_1 B_2 + B_1 D_2 \\ \text{---} & \text{---} \end{bmatrix}$$

$$\therefore V_1 = A V_3 + B I_3 \quad \text{---} \quad (1)$$

$$I_1 = C V_3 + D I_3$$

$$V_3 = \frac{V_1}{A} \quad \text{or} \quad V_3 = \frac{C}{I_1}$$

$$V_3 = \frac{V_1}{A_1 A_2 + B_1 C_2} = V_T$$



From ① when  $V_1 = 0$


$$AV_3 = -BI_3$$

$$\therefore \frac{V_3}{-I_3} = R_M = \frac{B}{A} = \frac{A_1 B_2 + B_1 D_2}{A_1 A_2 + B_1 C_2}$$

The connection of two 2-port networks is shown in the figure. The ABCD parameters of  $N_1$  and  $N_2$  networks are given as

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix}_{N_1} = \begin{bmatrix} 1 & 5 \\ 0 & 1 \end{bmatrix} \text{ and}$$
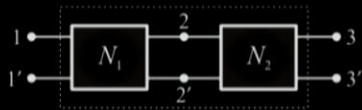
$$\begin{bmatrix} A & B \\ C & D \end{bmatrix}_{N_2} = \begin{bmatrix} 1 & 0 \\ 0.2 & 1 \end{bmatrix}$$



The ABCD parameters of the combined 2-port network are


(A)  $\begin{bmatrix} 2 & 5 \\ 0.2 & 1 \end{bmatrix}$       (B)  $\begin{bmatrix} 1 & 2 \\ 0.5 & 1 \end{bmatrix}$

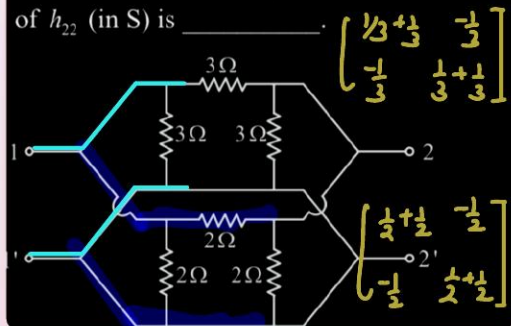(C)  $\begin{bmatrix} 5 & 2 \\ 0.5 & 1 \end{bmatrix}$       (D)  $\begin{bmatrix} 1 & 2 \\ 0.5 & 5 \end{bmatrix}$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & 5 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 0.2 & 1 \end{bmatrix} \\ = \begin{bmatrix} 2 & 5 \\ 0.2 & 1 \end{bmatrix} \quad (A)$$



In the h-parameter model of the 2-port network given in the figure shown, the value of  $h_{22}$  (in S) is \_\_\_\_\_.



Rule: Y parameters can be added

$$Y = \begin{bmatrix} \frac{2}{3} + 1 & -\frac{5}{6} \\ -\frac{5}{6} & \frac{2}{3} + 1 \end{bmatrix}$$

$$[Y] = \begin{bmatrix} 5/3 & -5/6 \\ -5/6 & 5/3 \end{bmatrix}$$

$$I_1 = 5/3 V_1 - 5/6 V_2 \quad (1)$$

$$I_2 = -5/6 V_1 + 5/3 V_2 \quad (2)$$

$$\frac{5}{6} V_2 = \frac{5}{3} V_1$$


$$V_1 = 0.5 V_2$$

Subs in (2)

$$I_2 = -\frac{5}{6} \left( \frac{1}{2} V_2 \right) + \frac{5}{3} V_2 = -\frac{5}{12} V_2 + \frac{20}{12} V_2 = \frac{15}{12} V_2$$


$$h_{22} = \frac{I_2}{V_2} = \frac{15}{12}$$

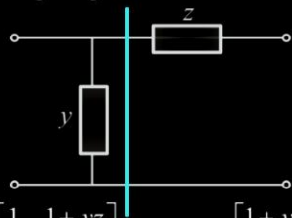Which one of the following is the transmission matrix for the network shown in the figure given below?




- (A)  $\begin{bmatrix} 1 & 1+yz \\ y & z \end{bmatrix}$  (B)  $\begin{bmatrix} 1+yz & z \\ y & 1 \end{bmatrix}$   
☒ (C)  $\begin{bmatrix} 1 & z \\ y & 1+yz \end{bmatrix}$  (D)  $\begin{bmatrix} 1 & 1+yz \\ z & y \end{bmatrix}$

ABCD

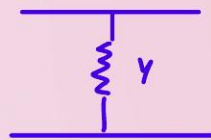

$$\begin{bmatrix} 1 & z \\ 0 & 1 \end{bmatrix}$$
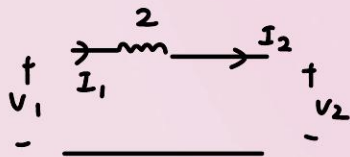
$$\begin{bmatrix} 1 & 0 \\ y & 1 \end{bmatrix}$$



$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

$$I_1 = I_2 \quad (1)$$

$$V_1 - z I_2 = V_2$$


$$V_1 = V_2 + z I_2 \quad (2)$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} 1 & z \\ 0 & 1 \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

In the arrangement of figure given below

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} 30 & 23 \\ 13 & 10 \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

ABCD parameter of Network  $N_0$  is

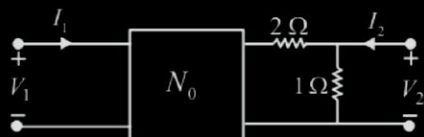

- (A)  $\begin{bmatrix} 7 & -9 \\ 3 & -4 \end{bmatrix}$  (B)  $\begin{bmatrix} 7 & 9 \\ 3 & 4 \end{bmatrix}$   
 (C)  $\begin{bmatrix} -7 & 9 \\ 3 & -4 \end{bmatrix}$  (D)  $\begin{bmatrix} 1 & 2 \\ 3 & 4 \end{bmatrix}$

$$\begin{bmatrix} 30 & 23 \\ 13 & 10 \end{bmatrix} = \begin{bmatrix} a & b \\ c & d \end{bmatrix} \begin{bmatrix} 1 & 2 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 1 & 1 \end{bmatrix}$$

$$\begin{bmatrix} 30 & 23 \\ 13 & 10 \end{bmatrix} = \begin{bmatrix} a & b \\ c & d \end{bmatrix} \begin{bmatrix} 3 & 2 \\ 1 & 1 \end{bmatrix} = \begin{bmatrix} \underline{3a+b} & \underline{2a+b} \\ \underline{3c+d} & \underline{2c+d} \end{bmatrix}$$

$$a = 30 - 23 = 7$$

$$b = 9$$

$$c = 13 - 10 = 3$$

$$d = 4$$

$$\begin{bmatrix} 7 & 9 \\ 3 & 4 \end{bmatrix} \quad (B)$$