

Chapter 3
DC Transients
Lecture 2

Switching at $t = 0$

$$v(t) = v(\alpha) + (v(\alpha^+) - v(\alpha)) e^{-t/\tau} \quad \text{if } t \geq 0$$

$$i(t) = i(\infty) + (i(0) - i(\infty)) e^{-t/\tau} ; \quad t \geq 0$$



$$i_C(t) = i_C(\infty) + (i_C(0^+) - i_C(\infty)) e^{-t/\tau}$$

$$= 0 + \left(\frac{V}{R} - 0 \right) e^{-t/\tau}$$

$$\tau = \text{Req } C$$

$$\tau = R_C$$

$$\therefore i_C(t) = \frac{V}{R} e^{-t/RC} \quad ; \quad t \geq 0$$

$\tau = RC$


Eq. R across C after SW

$$v_c(t) = v_c(\infty) + (v_c(0^+) - v_c(\infty)) e^{-t/\tau}$$


$$= V + (V - 0) e^{-t/\tau}$$

$$V_C(t) = \frac{V(1 - e^{-t/\tau})}{\tau = RC}; t \geq 0$$
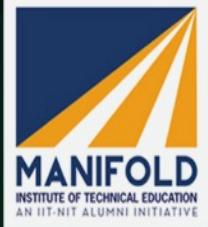
$$\therefore i_C(t) = -v/R e^{-t/\tau} ; t \geq 0$$



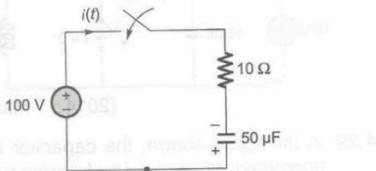In the circuit shown below, the initial charge on the capacitor is 2.5 mC , with the voltage polarity as indicated. The switch is closed at time $t = 0$. The current $i(t)$ at a time t after the switch is closed is




- (a) $i(t) = 15 \exp(-2 \times 10^3 t)$ A
 (b) $i(t) = 5 \exp(-2 \times 10^3 t)$ A
 (c) $i(t) = 10 \exp(-2 \times 10^3 t)$ A
 (d) $i(t) = -5 \exp(-2 \times 10^3 t)$ A

$$\therefore i(10t) = \frac{100 + 50}{10} = \underline{\underline{15A}}$$

$$\begin{aligned} t = 0^- & \quad g = CV \\ \therefore V = g/C & \quad \therefore V_C(0^-) = \frac{2.5mc}{50\mu F} \\ & = \frac{2500}{50} V \\ V_C(0^+) & = V_C(0^-) = 50V \\ & = \underline{\underline{50V}} \end{aligned}$$

$$V_1(0^+) = V_C(0^-) = 50\text{V}$$

$$t = \sigma^k$$

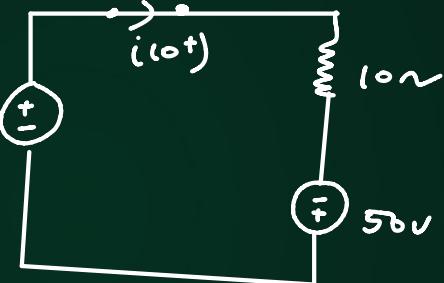

$t = \alpha$: ss after sw

$$\frac{Q}{Cap} \Rightarrow 0 < \quad \therefore i(\alpha) = 0$$

$$T = R_{eq}C = (10)(50\mu) = 500\mu$$


$$= \underline{0.5M}$$

$$\therefore i(t) = i(\alpha) + (i(\sigma t) - i(\alpha))e^{-t/\tau} \quad j \neq 0$$


$$i(t) = i(0^+) e^{-kt} \quad ; \quad t \geq 0$$

$$i(t) = 15 e^{-t/\tau} + z_0$$

$$i(t) = 15 e^{-2000t} ; t \geq 0$$

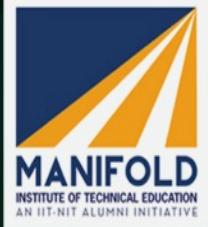


First order RL Circuit

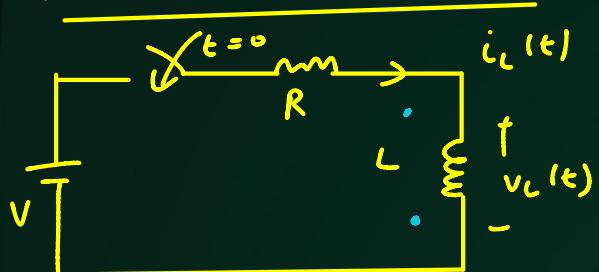


$$t = 0^- \quad i_L(0^-) = 0A$$
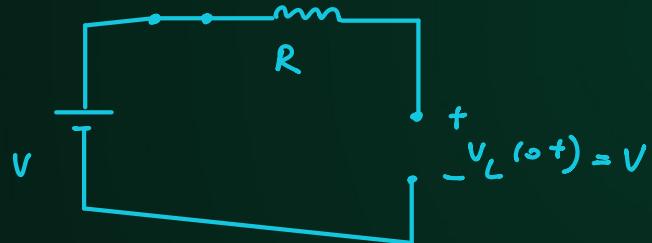
$$t = \underline{o^+} \quad i_C(o^+) = i_C(o^-) = OA$$



RL Circuit

$t = \alpha$ \downarrow ss after sw

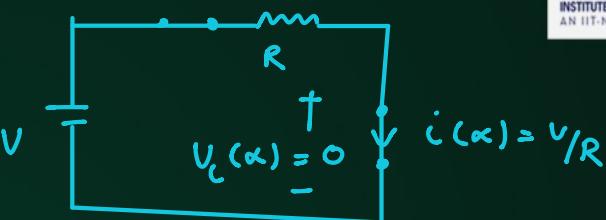

$$i_L(t) \rightarrow 0 \rightarrow v_R$$

$$v_c(t) \rightarrow v \neq 0$$


$$i_L(t) = \frac{V}{R} (1 - e^{-t/\tau}) \quad t \geq 0$$

$$V_L(t) = V e^{-t/\tau} \quad ; \quad t \geq 0$$

$$= \frac{L}{R_{eq}} = \frac{L}{R}$$

Find Time Constant

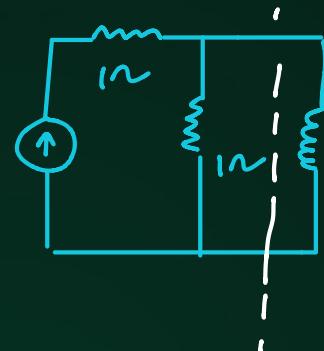i)  $R_{eq} = \frac{1}{2} \Omega$
 $T = \frac{C}{R_{eq}} = \frac{1}{0.5} = 2 \text{ sec}$ (A)




$$T = \frac{L}{R_{eq}} = \frac{1}{1} = 1 \text{ sec}$$


3)

$$T = R_{eq} C = 2(1) = \underline{2 \text{ sec}}$$


Q) Find the time constant

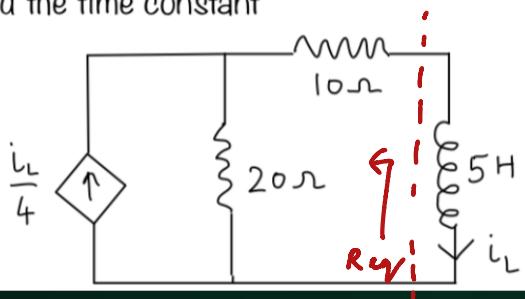
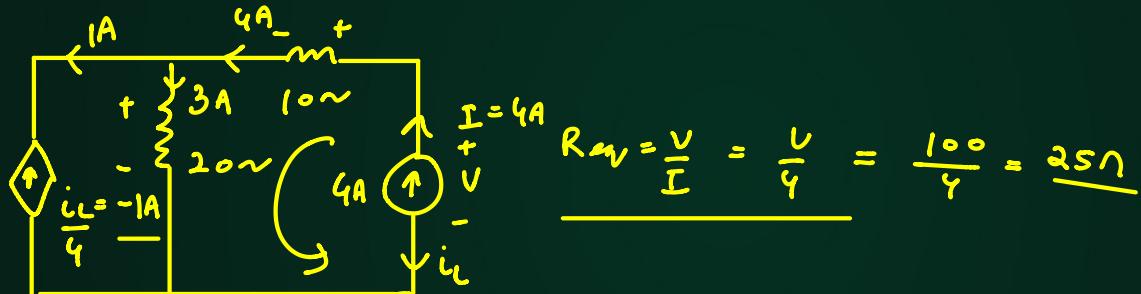
$$T = \frac{L}{R_{AV}} = \frac{5}{25} = \underline{\underline{0.2 \text{ sec}}}$$


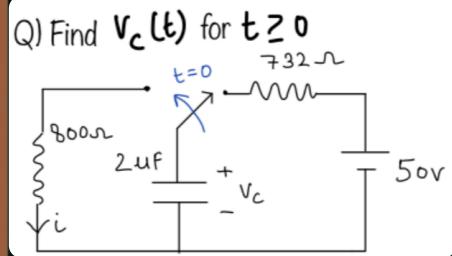
$$i_L = -4A \quad V = (4)(10) + (3)(20) = 100V$$



$$V_C(t) = V_C(0^+) e^{-t/\tau} ; t \geq 0 \quad (\text{Source Free})$$

$$V_C(0^-) = V_C(0^+)$$


$$\underline{t=0^-} : V_C(0^-) : \underline{\text{SS bfr SW}}$$

$$\therefore V_C(0^-) = 50V$$

$$V_C(t) = 50 e^{-t/\tau} ; t \geq 0 \quad \tau = R_{\text{eq}} C \\ = (0.8k)(2\mu) = \underline{\underline{1.6ms}}$$

$$V_C(t) = 50 e^{-\frac{1000t}{1.6}} ; t \geq 0$$

Q) Find $v_s (o^+)$

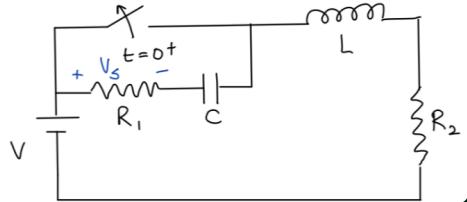


$$\begin{array}{l} V_C(=0) \\ I_L(=0) \end{array}$$

$$\underline{t=0^-} : \underline{\underline{ss \ bfr \ sw}}_{i,i=}$$

A circuit diagram showing a voltage source V in series with resistor R_1 . The output voltage $V_c(0^-)$ is labeled as $0V$.

$$t = 0^+$$

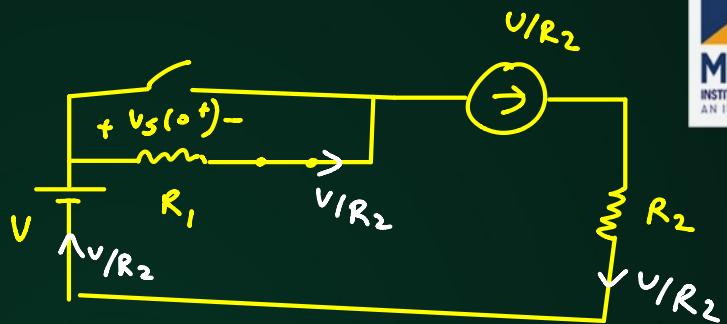

$$V_S(-+) = \left(\frac{V}{R_2}\right) (R_1)$$